

AN-1357 LM2744 Evaluation Board

1 Introduction

This application note describes the LM2743 printed circuit board (PCB) design and provides an example typical application circuit. The demo board allows component design flexibility in order to demonstrate the versatility of the LM2744 IC.

The demo board contains a voltage-mode, high-speed synchronous buck regulator controller with an external adjustable reference voltage between 0.5V and 1.5V. The demo board design incorporates the LM4140 high precision low noise reference IC providing 1.0V to the reference pin (V_{REF}). Though the control sections of the IC are rated for 3 to 6V (V_{CC}), the driver sections are designed to accept input supply rails (V_{IN}) as high as 14V. It operates at a fixed-frequency, adjustable from 50 kHz to 1 MHz with one external resistor.

The demo board design regulates to an output voltage of 1.2V at 3.5A with a switching frequency of 1MHz. Note, the demo board is optimized for a 1MHz, 14V input voltage compensation design; if another switching frequency and input voltage is desired, please consult the LM2744 data sheet for control loop compensation procedures. For additional design modifications refer to the Design Consideration section of the *LM2744 Low Voltage N-Channel MOSFET Synchronous Buck Regulator Controller with External Reference* [SNVS292](#) data sheet.

2 Additional Footprints

A Schottky diode footprint (D1) is available in parallel to the low side MOSFET. This component can improve efficiency, due to the lower forward drop than the low side MOSFET body diode conducting during the anti-shoot through period. Select a Schottky diode that maintains a forward drop around 0.4 to 0.6V at the maximum load current (consult the I-V curve). In addition select the reverse breakdown voltage to have sufficient margin above the maximum input voltage.

Footprint C13 is available for a multilayer ceramic capacitor (MLCC) connected as close as possible to the source of the low side MOSFET and drain of the high side MOSFET. This will provide low supply impedance to the high speed switch currents, thus minimizing the input supply noise. For example; a MLCC is used (C13) in combination with aluminum electrolytic input filter capacitors, placed in designators C12 and C14, because MLCC have lower impedance than electrolytics. If MLCCs are used in designators C12 and C14 component C13 is not necessary.

The PCB is designed on two layers with 1oz. copper on a 62mil FR4 laminate.

3 Guidelines for Additional Options

When using a DC power supply to set a reference voltage (V_{REF}), connect a capacitor (C20) from V_{DCS} to GND to filter the DC power supply. A good starting point is 10 μ F, but may need to be varied depending on the magnitude of the DC power supply noise (any make of capacitor will do as long as the capacitance is maintained within the operating temperature range). Remove R10 and place a zero ohm jumper in designator R12.

Designators R12 and R13 are provided for DDR SDRAM (double data rate synchronous dynamic random access memory) active termination design. Set V_{REF} to half the DDR supply voltage by using designators R12 and R13 as a voltage divider. Remove resistors R7, R10 and capacitor C21, and connect the DDR supply voltage rail to terminal V_{DCS} , refer to [Figure 2](#). The modified circuit in [Figure 1](#) can sink or source current in excess of 3A – a load transient response applied to the output of [Figure 2](#) is provided in [Figure 3](#).

All trademarks are the property of their respective owners.

Do not exceed 5.6V on the VCC pin of the demo board. The board layout connects together both the input voltage of the LM4140-1.0 (pin 2) and the control section of the LM2744 (VCC). The maximum DC supply voltage for the control section of the LM2744 is 6V, while 5.6V is the maximum rating for any input pin of the LM4140. If the design requires the control section of the LM2744 to be 6V, a shunt zener reference may be placed at designator location (D3) to maintain the input voltage of the LM4140 between 1.8V and 5.5V. The cathode of the zener is connected to the input of the LM4140 and the anode to GND. The resistance of R10 must be selected to supply the appropriate amount of biasing current into the zener and the LM4140 (refer to the Electrical Characteristic table of the *LM4140 High Precision Low Noise Low Dropout Voltage Reference* [LM4140](#) data sheet).

4 Typical Application Circuit

The typical application circuit in [Figure 1](#) provides the component designators used on the demo board.

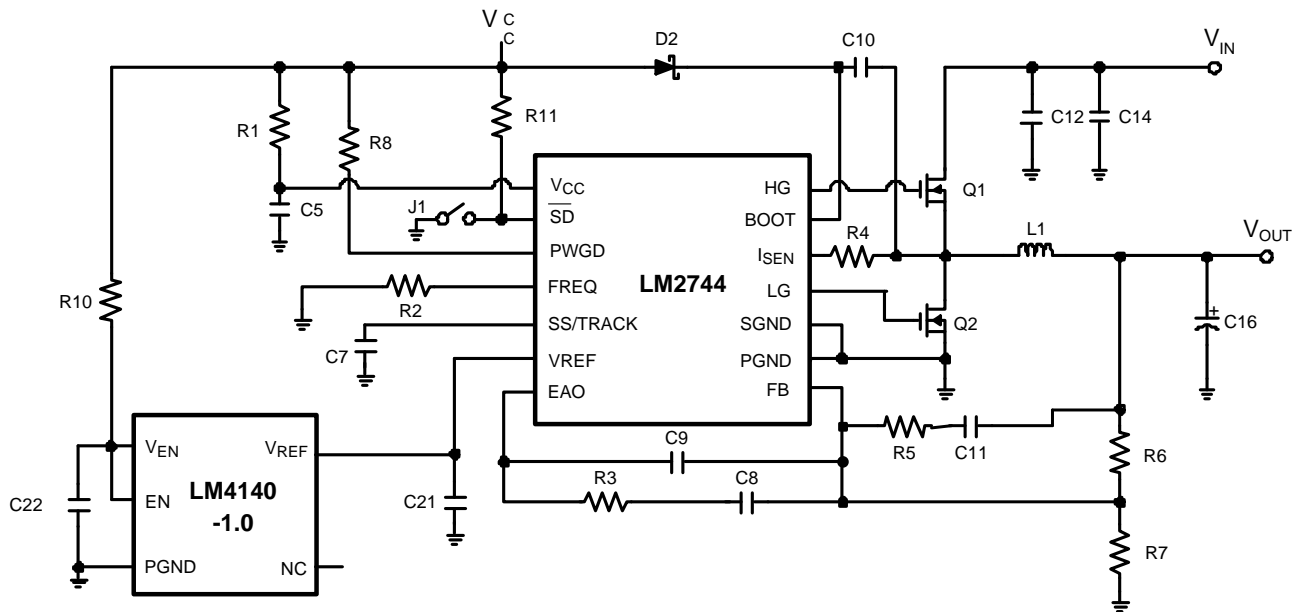


Figure 1. Typical Application

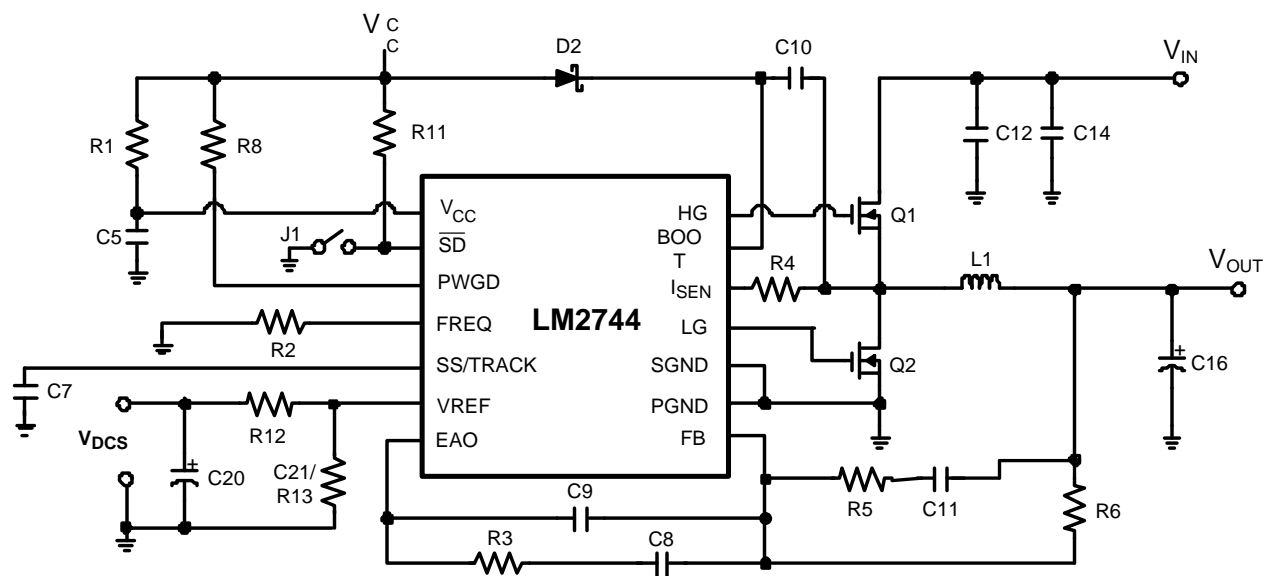


Figure 2. DDR SDRAM Termination Supply

5 Performance Characteristics

5.1 Load Transient Response

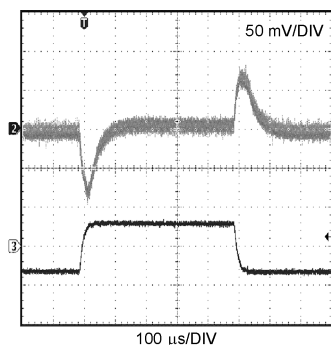


Figure 3. $\pm 3A$ Load Transient Response Applied to circuit in [Figure 2](#)
($V_{IN} = V_{CC} = 3.3V$ and $V_{OUT} = 1.2V$).
CH 2 - V_{OUT} AC coupled and CH 3 - 5A/ DIV

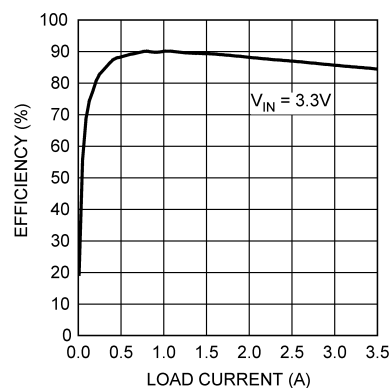


Figure 4. Efficiency vs. Load Current
 $V_{OUT} = 1.2V$, $f_{SW} = 1MHz$

5.2 Switch Node Voltage and Output Ripple Voltage

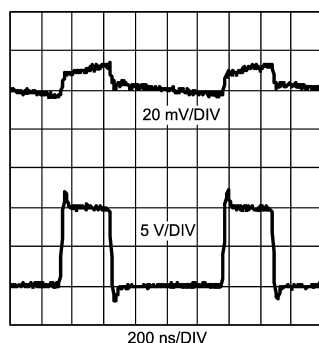


Figure 5. $V_{IN} = V_{CC} = 3.3V$,
 $V_{OUT} = 1.2V$,
 $I_{LOAD} = 0A$, $f_{SW} = 1MHz$.
20 MHz Bandwidth Limit

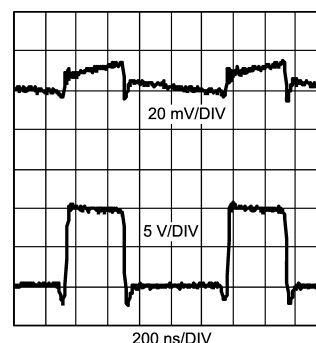


Figure 6. $V_{IN} = V_{CC} = 3.3V$,
 $V_{OUT} = 1.2V$,
 $I_{LOAD} = 3.5A$, $f_{SW} = 1MHz$.
20 MHz Bandwidth Limit

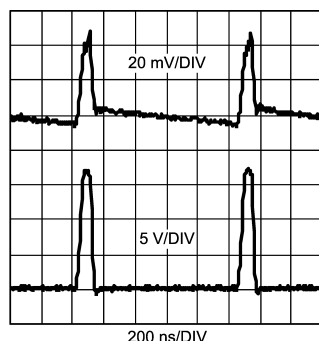


Figure 7. $V_{IN} = 14V$, $V_{CC} = 5V$,
 $V_{OUT} = 1.2V$, $I_{LOAD} = 0A$, $f_{SW} = 1MHz$.
20 MHz Bandwidth Limit

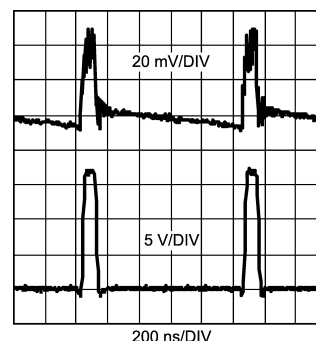
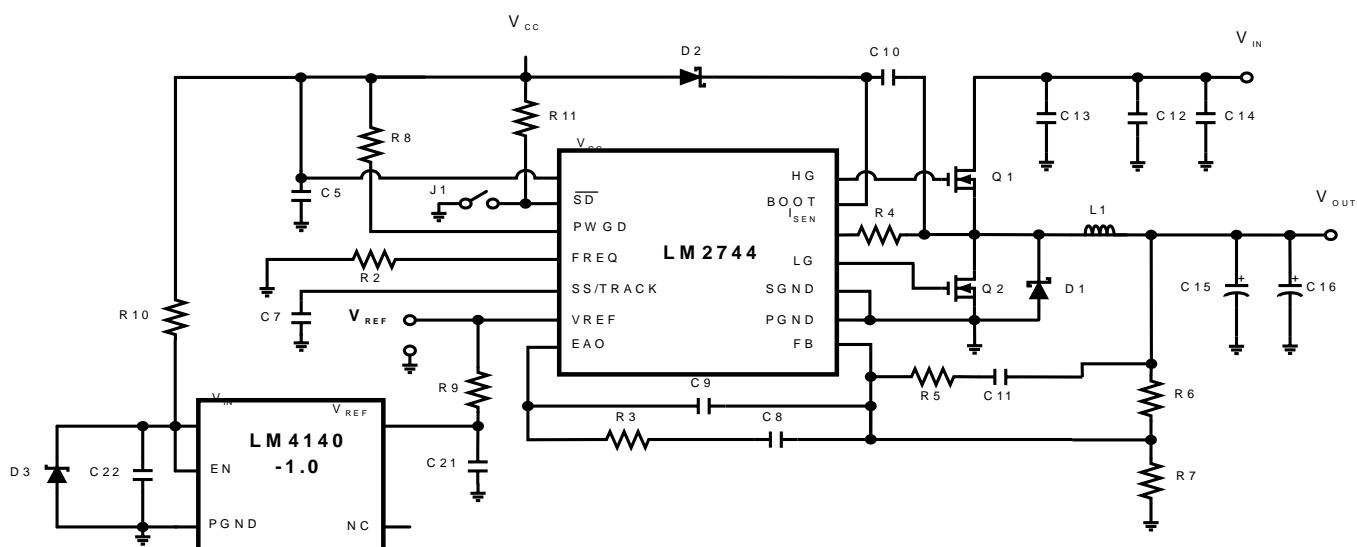


Figure 8. $V_{IN} = 14V$, $V_{CC} = 5V$,
 $V_{OUT} = 1.2V$, $I_{LOAD} = 3.5A$, $f_{SW} = 1MHz$.
20 MHz Bandwidth Limit

Table 1. Bill of Materials

Designator	Function	Part Description	Part Number
U1	Controller	IC LM2744 TSSOP14	Texas Instruments
U2	Low Dropout Reg	IC LM4140BCM-1.0 SOIC-8	Texas Instruments
C5	VCC Decoupling	Cer Cap 1 μ F 25V 10% 0805	Murata GRM216R61E105KA12B
C7	Soft Start Cap	Cer Cap 12nF 25V 10% 0805	Vishay VJ0805Y123KXX
C8	Comp Cap	Cer Cap 1.2nF 25V 10% 0805	Vishay VJ0805Y122KXX
C9	Comp Cap	Cer Cap 15pF 50V 10% 0805	Vishay VJ0805A150KAA
C10	Cboot	Cer Cap 0.1 μ F 25V 10% 0805	Vishay VJ0805Y104KXX
C11	Comp Cap	Cer Cap 1.8nF 25V 10% 0805	Vishay VJ0805Y182KXX
C12	Input Filter Cap	Cer Cap 10 μ F 25V 10% 1210	AVX 12103D106MAT
C14	Input Filter Cap	Cer Cap 10 μ F 25V 10% 1210	AVX 12103D106MAT
C16	Output Filter Cap	470 μ F, 6.3V, 10m ohm ESR POScap	Sanyo 6TPD470
C21	Reference Output Cap	Niobium Oxide Cap 4.7 μ F 6V	AVX NOJA475M0006R
C22	Reference Input Cap	Cer Cap 0.47 μ F 25V 10% 1206	Vishay VJ1206Y474KXX
R1	VCC Filter Res	Res 10 Ω .25W 0805	Vishay CRCW08051000F
R2	Frequency Adjust Res	Res 24.9K Ω .25W 0805	Vishay CRCW08052492F
R3	Comp Res	Res 21K Ω .25W 0805	Vishay CRCW08052102F
R4	Current Limit Res	Res 3.16K Ω .25W 0805	Vishay CRCW08053161F
R5	Comp Res	Res 2.94K Ω .25W 0805	Vishay CRCW08052941F
R6	Res Divider, upper	Res 10.0K Ω .25W 0805	Vishay CRCW08051002F
R7	Res Divider, lower	Res 59K Ω .25W 0805	Vishay CRCW08055902F
R8	PWGD Pull-Up	Res 100K Ω .25W 0805	Vishay CRCW08051003F
R10	Zero Ohm	Res 0 Ω 0805	Vishay CRCW08050000
R11	Shut Down Pull-Up	Res 100K Ω .25W 0805	Vishay CRCW12061003F
D2	Bootstrap Diode	Schottky Diode, SOD-123	MBR0530LTI
L1	Output Filter Inductor	Inductor 1 μ H, 5.3Arms, 10.2m Ω	Cooper DR73-1R0
Q1-Q2	Top and Bottom FETs	Dual N-MOSFET, V_{DS} = 20V, 24m Ω at 2.5V	Vishay 9926BDY


Figure 9. Complete Demo Board Schematic

6 PCB Layout Diagram(s)

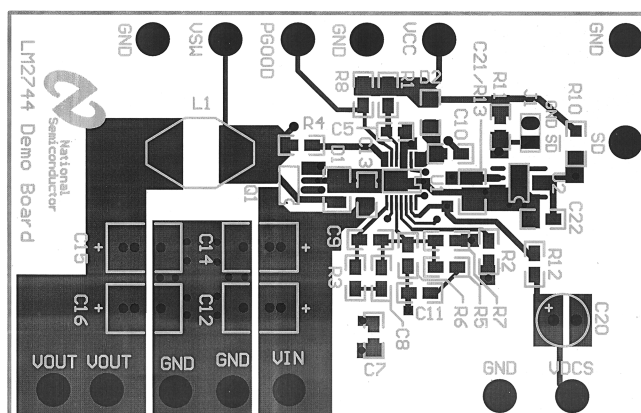


Figure 10. Top Layer and Top Overlay

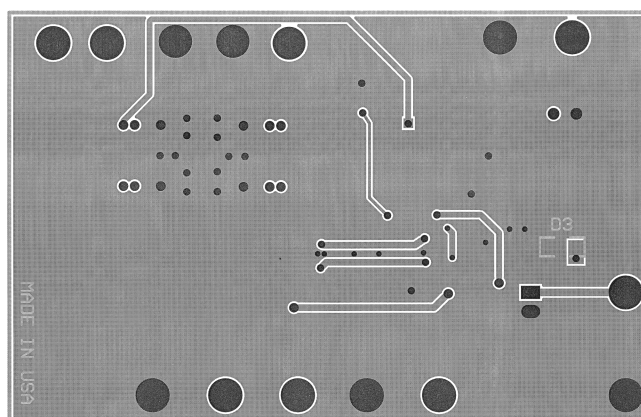


Figure 11. Bottom Layer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com