

Single-chip Type with Built-in FET Switching Regulators

High-efficiency Step-up Switching Regulator with Built-in Power MOSFET





BD8314NUV No.13027EET09

Description

ROHM's High-efficiency Step-up Switching Regulator Built-in Power MOSFET BD8314NUV generates step-up output including 8 V or 10 V from 4 batteries, batteries such as Li1cell or Li2cell etc. or a 5 V fixed power supply line.

This IC allows easy production of small and a wide range of output current, and is equipped with an external coil/capacitor downsized by high frequency operation of 1.2 MHz, built-in 2.5 A rated 80 m Ω Nch FET SW, and flexible phase compensation system on board.

Features

- 1) Incorporates Nch FET capable of withstanding 2.5 A/14 V.
- 2) Incorporates phase compensation device between input and output of ERROR AMP.
- 3) Small coils and capacitors to be used by high frequency operation of 1.2 MHz
- 4) Input voltage 3.0 V ~ 12 V
- 5) Output current 600 mA (3.5 V ~ 10 V) at 10 V 600 mA (3.0 V ~ 8 V) at 8 V
- 6) Incorporates soft-start function.
- 7) Incorporates timer latch system short protecting function.
- 8) As small as 3 mm × 3 mm, SON 10-pin package VSON010V3030

Application

General portable equipment like DSC/DVC powered by 4 dry batteries or Li2cell

Absolute Maximum Ratings

Parameter	Symbol	Ratings	Unit
Maximum applied power voltage	VCC, LX	14	V
Maximum input voltage	SWOUT, INV	14	V
Maximum input current	linmax	2.5	Α
Power dissipation	Pd	700*	mW
Operating temperature range	Topr	-25 to +85	°C
Storage temperature range	Tstg	-55 to +150	°C
Junction temperature	Tjmax	+150	°C

^{*} When used at Ta = 25°C or more installed on a $74.2 \times 74.2 \times 1.6^{t}$ mm board, the rating is reduced by 5.6 mW/°C.

Operating Conditions (Ta = 25°C)

Parameter	Symbol	Ratings	Unit
Power supply voltage	VCC	3.0 to 12	V
Output voltage	VOUT	4.0 to 12	V

●Electrical Characteristics

(Unless otherwise specified, Ta = 25 °C, VCC = 7.4 V)

Parameter			Limits			l loit	0 1:::
		Symbol	Min.	Тур.	Max.	Unit	Conditions
[Low voltage input i	malfunction prev	enting circuit]					
Detection threshold voltage		Vuv	-	2.4	2.6	V	VREG monitor
Hysteresis range		ΔVυvhy	50	100	200	mV	
[Oscillator]							
Oscillation frequence	су	fosc	1.1	1.2	1.3	MHz	
[Regulator]							
Output voltage		VREG	4.65	5.0	5.35	V	
[ERROR AMP]							
INV threshold voltage		VINV	0.99	1.00	1.01	V	
Input bias current		IINV	-50	0	50	nA	Vcc=11.0V , VINV=5.5V
Soft-start time		Tss	5.3	8.8	12.2	msec	
[PWM comparator]							
LX Max Duty		Dmax1	77	85	93	%	
[SWOUT]							
ON resistance		Ronswout	-	50	100	Ω	
[Output]							
LX NMOS ON resis	stance	Ron	-	80	150	mΩ	
LX leak current		lleak	-1	0	1	μΑ	
[STB]							
STB pin	Operation	VsтвН	2.5	-	VCC	V	
control voltage	No-operation	VSTBL	-0.3	-	0.3	V	
STB pin pull-down resistance		Rstb	250	400	700	kΩ	
[Circuit current]						•	
Standby current VC	C	Ізтв	-	-	1	μA	
Circuit current at operation VCC		Icc	-	600	900	μΑ	VINV=1.2V

Description of Pins

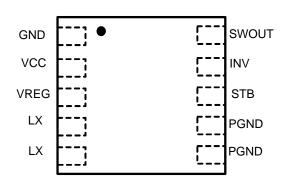


Fig.1 Pin layout

Pin No.	Pin Name	Function
1	GND	Ground terminal
2	VCC	Control part power input terminal
3	VREG	5 V output terminal of regulator for internal circuit
4~5	Lx	Coil connecting terminal
6~7	PGND	Power transistor ground terminal
8	STB	ON/OFF terminal
9	INV	ERROR AMP input terminal
10	SWOUT	STBSW for split resistance

●Block Diagram

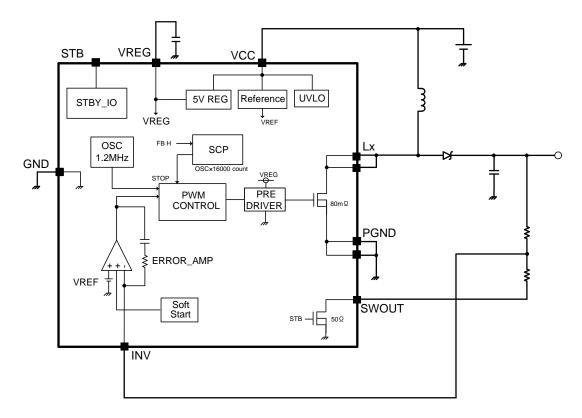


Fig.2 Block diagram

Description of Blocks

1. VREF

This block generates ERROR AMP reference voltage.

The reference voltage is 1.0 V.

UVLO

Circuit for preventing low voltage malfunction

Prevents malfunction of the internal circuit at activation of the power supply voltage or at low power supply voltage. Monitors VREG pin voltage to turn off all output FET and DC/DC converter output when VREG voltage is lower than 2.4 V, and reset the timer latch of the internal SCP circuit and soft-start circuit. This threshold contains 100 mV hysteresis.

3. SCP

Timer latch system short-circuit protection circuit

When the INV pin is the set 1.0 V or lower voltage, the internal SCP circuit starts counting. The internal counter is in synch with OSC; the latch circuit activates after a lapse of 13.3 msec after the counter counts about 16000 oscillations and then, turn off DC/DC converter output. To reset the latch circuit, turn off the STB pin once. Then, turn it on again or turn on the power supply voltage again.

OSC

Circuit for oscillating saw tooth waves with an operation frequency fixed at 1.2 MHz

5. ERROR AMP

Error amplifier for detecting output signals and outputting PWM control signals

The internal reference voltage is set at 1.0 V.

A primary phase compensation device of 200 pF, 62 k Ω is built in between the inverting input terminal and the output terminal of this ERROR AMP.

6. PWM COMP

Voltage-pulse width converter for controlling output voltage corresponding to input voltage

Comparing the internal SLOPE waveform with the ERROR AMP output voltage, PWM COMP controls the pulse width to the output to the driver.

Max Duty is set at 85%.

SOFT START

Circuit for preventing in-rush current at startup by bringing the output voltage of the DC/DC converter into a soft-start Soft-start time is in synch with the internal OSC, and the output voltage of the DC/DC converter reaches the set voltage after about 10000 oscillations.

8. PRE DRIVER

CMOS inverter circuit for driving the built-in Nch FET.

a STRV IO

Voltage applied on STB pin (8 pin) to control ON/OFF of IC

Turned ON when a voltage of 2.5 V or higher is applied and turned OFF when the terminal is open or 0 V is applied. Incorporates approximately 400 k Ω pull-down resistance.

10. Nch FET SW

Built-in SW for switching the coil current of the DC/DC converter. Incorporates an 80 m Ω NchFET SW capable of withstanding 14 V. Since the current rating of this FET is 2.5 A, it should be used within 2.5 A including the DC current and ripple current of the coil.

● Reference Data (Unless otherwise specified, Ta = 25°C, VCC = 7.4 V)

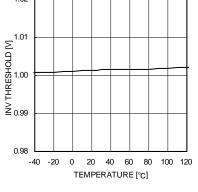


Fig.3. INV threshold temperature property

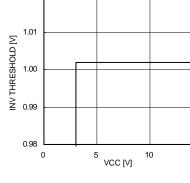


Fig.4. INV threshold power supply property

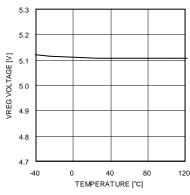


Fig.5. VREG output temperature property

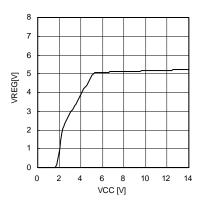


Fig.6. VREG output power supply property

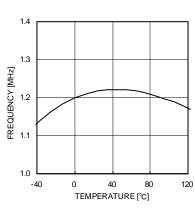


Fig.7. fosc temperature property

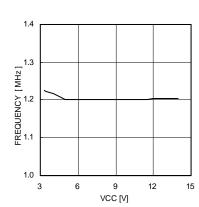


Fig.8. fosc voltage property

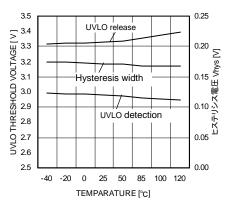


Fig.9. UVLO threshold temperature property

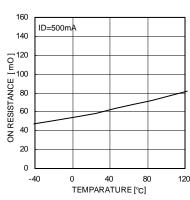


Fig.10. Nch FET ON resistance temperature property

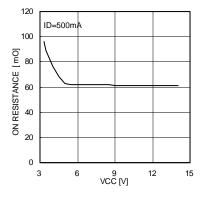


Fig.11. Nch FET ON resistance power supply property

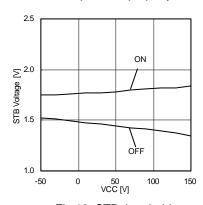


Fig.12. STB threshold temperature property

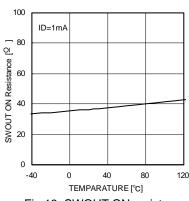


Fig.13. SWOUT ON resistance temperature property

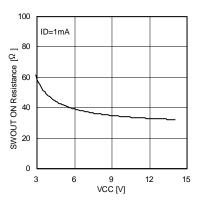


Fig.14. SWOUT ON resistance power supply property

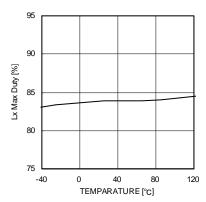


Fig.15. Lx Max duty temperature property

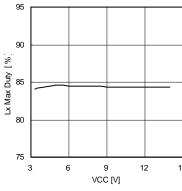


Fig.16. Lx Max duty power supply property

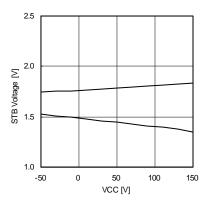


Fig.17. Circuit current temperature property

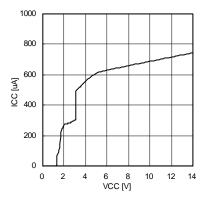


Fig.18. Circuit current power supply property

● Example of Application Input: 3.0 to 10 V, output: 10 V / 500 mA

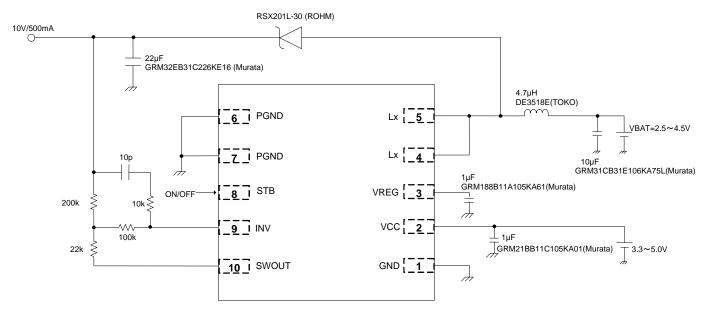


Fig.19 Reference application diagram

Reference Application Data 1

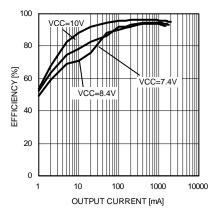


Fig.20 Power conversion efficiency 1

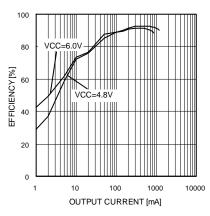


Fig.21 Power conversion efficiency 2

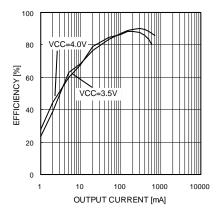


Fig.22 Power conversion efficiency 3

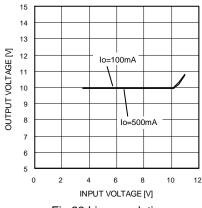


Fig.23 Line regulation

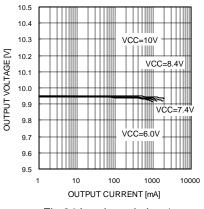


Fig.24 Load regulation 1



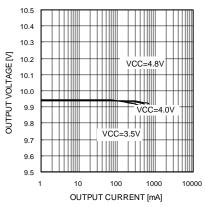


Fig.25 Load regulation 2

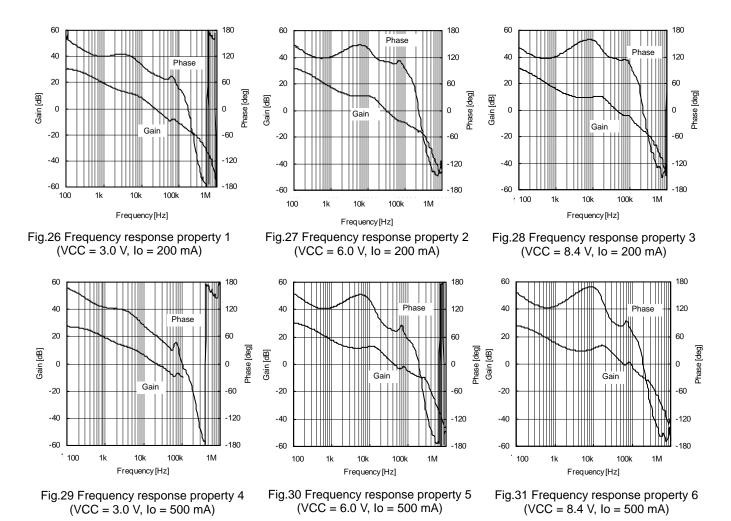● Reference Application Data 2 (VCC = 3.0 V, 6.0 V, 8.4 V, VOUT = 10 V)



● Reference Board Pattern

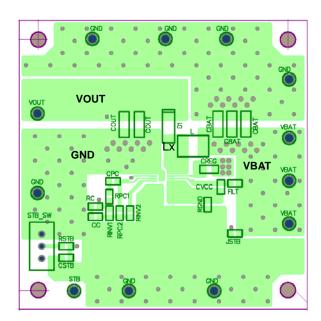

- The radiation plate on the rear should be a GND flat surface of low impedance in common with the PGND flat surface.
- It is recommended to install a GND pin in another system as shown in the drawing without connecting it directly to this PGND

●Limits of the lowest power supply voltage to start up

When using configuration of inputting VCC voltage from output voltage of DC/DC converter, the input voltage as power supply for the IC drops by Vf voltage of external Diode.

The worst condition is shown as below.

VCC terminal voltage - Vf voltage of external diode ≥ the worst voltage of UVLO reset voltage(=2.8V)

Please judge this IC is useable or not considering needed start up voltage and load current.

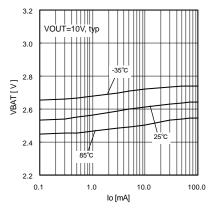


Fig.32 start up voltage Vs load current

Selection of Part for Applications

(1) Inductor

A shielded inductor that satisfies the current rating (current value, Ipeak as shown in the drawing below) and has a low DCR (direct resistance component) is recommended.

Inductor values affect inductor ripple current, which will cause output ripple.

Ripple current can be reduced as the coil L value becomes larger and the

switching frequency becomes higher.

Ipeak = IOUT ×
$$(VOUT / VIN) / \eta + \Delta IL / 2[A]$$
 · · · (1)

$$\Delta IL = \frac{VIN}{L} \times \frac{VOUT - VIN}{VOUT} \times \frac{1}{f} [A]$$
 (2)

(η: Efficiency, ΔIL: Output ripple current, f: Switching frequency)

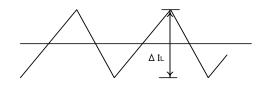


Fig.33 Inductor current

As a guide, inductor ripple current should be set at about 20 to 50% of the maximum input current.

* Current over the coil rating flowing in the coil brings the coil into magnetic saturation, which may lead to lower efficiency or output oscillation. Select an inductor with an adequate margin so that the peak current does not exceed the rated current of the coil.

(2) Output capacitor

A ceramic capacitor with low ESR is recommended for output in order to reduce output ripple.

There must be an adequate margin between the maximum rating and output voltage of the capacitor, taking the DC bias property into consideration.

Output ripple voltage is obtained by the following equation.

$$VPP = IOUT \times \frac{VOUT - VIN}{f \times CO \times VOUT} + IOUT \times RESR[V]$$
 (3)

Setting must be performed so that output ripple is within the allowable ripple voltage.

(3) Output voltage setting

The internal reference voltage of the ERROR AMP is 1.0 V. Output voltage is obtained by Equation (4) of Fig. 33, but it should be designed taking about 50 Ω , an error of NMOS ON resistance of SWOUT into consideration.

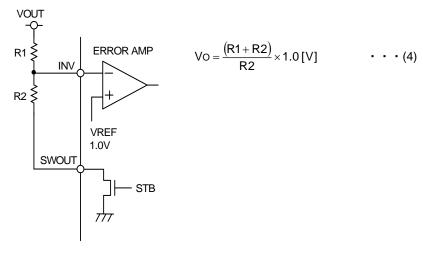


Fig.34 Setting of voltage feedback resistance

(4) DC/DC converter frequency response adjustment system

Condition for stable application

The condition for feedback system stability under negative feedback is that the phase delay is 135 °or less when gain is 1 (0 dB).

Since DC/DC converter application is sampled according to the switching frequency, the bandwidth GBW of the whole system (frequency at which gain is 0 dB) must be controlled to be equal to or lower than 1/10 of the switching frequency.

In summary, the conditions necessary for the DC/DC converter are:

- Phase delay must be 135° or lower when gain is 1 (0 dB).
- Bandwidth GBW (frequency when gain is 0 dB) must be equal to or lower than 1/10 of the switching frequency.

To satisfy above two items, R₁, R₂, R₃, C_S and R_S in Fig. 35 should be set as follows.

[1] R₁, R₂, R₃

BD8314NUV incorporates phase compensation devices of R4=62 $k\Omega$ and C2=200pF. These C2 and R₁, R₂, and R₃ values decide the prim ary pole that determines the bandwidth of DC/DC converter.

Primary pole point frequency

fp=
$$\frac{1}{2\pi \left\{ A \times (\frac{R_1 \cdot R_2}{R_1 + R_2} + R_3) \times C_2 \right\}}$$
 ... (1)

DC/DC converter DC Gain

DC Gain =
$$A \times \frac{1}{B} \times \frac{Vout}{Vout - Vin}$$
 · · · · (2)

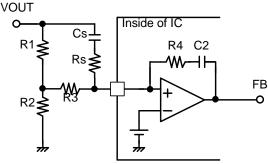


Fig.35 Example of phase compensation setting

A : ERROR AMP Gain About $100dB = 10^5$

B : Oscillator amplification = 0.5V

V_{IN} : Input voltage V_{OUT} : Output voltage

By Equations (1) and (2), the frequency f_{sw} of point 0 dB under limitation of the bandwidth of the DC gain at the primary pole point is as shown below.

$$fsw = fp \times DC \ Gain = \frac{1}{2\pi C2 \times \left(\frac{R_1 \cdot R_2}{R_1 + R_2} + R_3\right)} \times \frac{1}{B} \times \frac{Vout}{Vout - Vin} \cdot \cdot \cdot \cdot (3)$$

It is recommended that f_{sw} should be approx.10 kHz. When load response is difficult, it may be set at approx. 20 kHz. By this setting, R_1 and R_2 , which determine the voltage value, will be in the order of several hundred $k\Omega$. Therefore, if an appropriate resistance value is not available and routing may cause noise, the use of R_3 enables easy setting.

[2]Cs and Rs setting

In the step-up DC/DC converter, the secondary pole point is caused by the coil and capacitor as expressed by the following equation.

$$fLC = \frac{1 - D}{2\pi\sqrt{(LC)}} \cdot \cdot \cdot (4)$$

D: ON Duty =
$$(V_{OUT} - V_{IN}) / V_{OUT}$$

This secondary pole causes a phase rotation of 180°. To secure the stability of the system, put zero points in 2 places to perform compensation.

Zero point by built-in CR
$$fz_1 = \frac{1}{2\pi R_4 C_2} = 13 \text{ kHz}$$
 (5)

Zero point by Cs
$$fz_1 = \frac{1}{2\pi (R_1 + R_3)Cs} \qquad \cdot \cdot \cdot (6)$$

Setting C_S to be half to 2 times a frequency as large as f_{LC} provides an appropriate phase margin. It is desirable to set Rs at about 1/20 of (R_1+R_3) to cancel any phase boosting at high frequencies.

Those pole points are summarized in the figure below. The actual frequency property is different from the ideal calculation because of part constants. If possible, check the phase margin with a frequency analyzer or network analyzer, etc.. Otherwise, check for the presence or absence of ringing by load response waveform and also check for the presence or absence of oscillation under a load of an adequate margin.


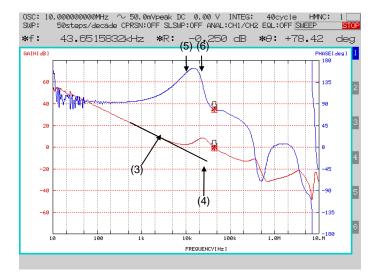


Fig. 36 Example of DC/DC converter frequency property (Measured with FRA5097 by NF Corporation)

●I/O Equivalence Circuit

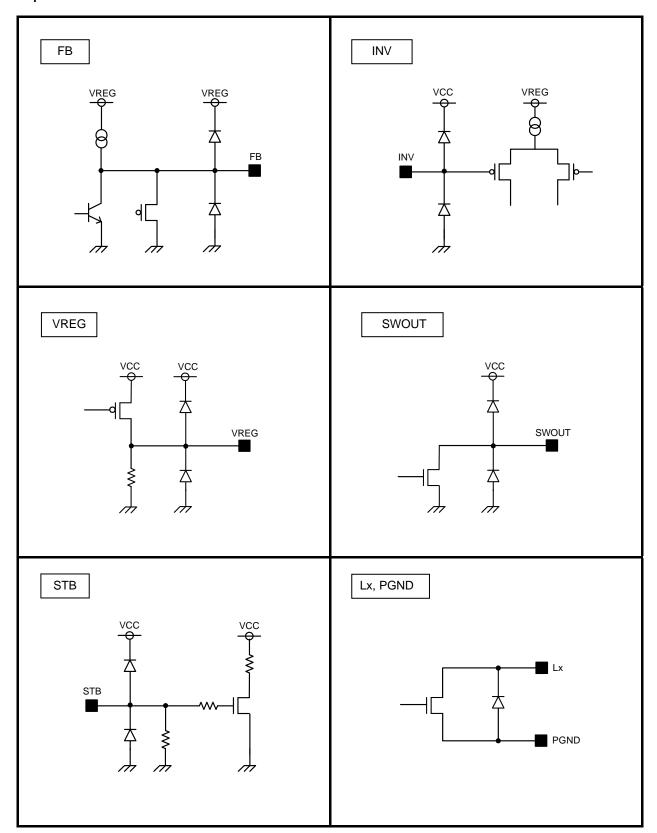

Notes for Use

1) Absolute Maximum Rating

We dedicate much attention to the quality control of these products, however the possibility of deterioration or destruction exists if the impressed voltage, operating temperature range, etc., exceed the absolute maximum ratings. In addition, it is impossible to predict all destructive situations such as short-circuit modes, open circuit modes, etc. If a special mode exceeding the absolute maximum rating is expected, please review matters and provide physical safety means such as fuses, etc.

2) GND Potential

Keep the potential of the GND pin below the minimum potential at all times.

Thermal Design

Work out the thermal design with sufficient margin taking power dissipation (Pd) in the actual operation condition into account.

4) Short Circuit between Pins and Incorrect Mounting

Attention to IC direction or displacement is required when installing the IC on a PCB. If the IC is installed in the wrong way, it may break. Also, the threat of destruction from short-circuits exists if foreign matter invades between outputs or the output and GND of the power supply.

5) Operation under Strong Electromagnetic Field

Be careful of possible malfunctions under strong electromagnetic fields.

6) Common Impedance

When providing a power supply and GND wirings, show sufficient consideration for lowering common impedance and reducing ripple (i.e., using thick short wiring, cutting ripple down by LC, etc.) as much as you can.

7) Thermal Protection Circuit (TSD Circuit)

This IC contains a thermal protection circuit (TSD circuit). The TSD circuit serves to shut off the IC from thermal runaway and does not aim to protect or assure operation of the IC itself. Therefore, do not use the TSD circuit for continuous use or operation after the circuit has tripped.

8) Rush Current at the Time of Power Activation

Be careful of the power supply coupling capacity and the width of the power supply and GND pattern wiring and routing since rush current flows instantaneously at the time of power activation in the case of CMOS IC or ICs with multiple power supplies.

9) IC Terminal Input

This is a monolithic IC and has P+ isolation and a P substrate for element isolation between each element. P-N junctions are formed and various parasitic elements are configured using these P layers and N layers of the individual elements. For example, if a resistor and transistor are connected to a terminal as shown on Fig.37:

OThe P-N junction operates as a parasitic diode

when GND > (Terminal A) in the case of a resistor or when GND > (Pin B) in the case of a transistor (NPN)

OAlso, a parasitic NPN transistor operates using the N layer of another element adjacent to the previous diode in the case of a transistor (NPN) when GND > (Pin B).

The parasitic element consequently rises under the potential relationship because of the IC's structure. The parasitic element pulls interference that could cause malfunctions or destruction out of the circuit. Therefore, use caution to avoid the operation of parasitic elements caused by applying voltage to an input terminal lower than the GND (P board), etc.



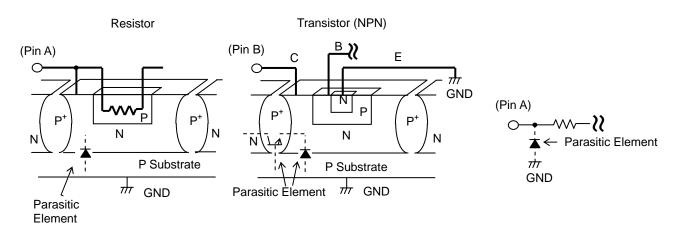



Fig.37 Example of simple structure of Bipolar IC

Ordering part number

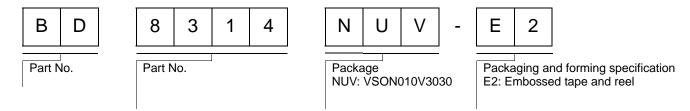

VSON010V3030

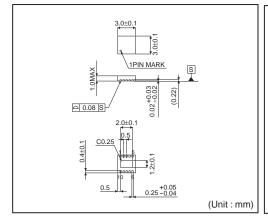

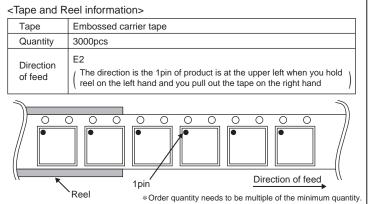

Notes

- 1) The information contained herein is subject to change without notice.
- Before you use our Products, please contact our sales representative and verify the latest specifications:
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors. Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Poducts beyond the rating specified by ROHM
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products are intended for use in general electronic equipment (i.e. AV/OA devices, communication, consumer systems, gaming/entertainment sets) as well as the applications indicated in this document.
- 7) The Products specified in this document are not designed to be radiation tolerant.
- 8) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative: transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 9) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 10) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 11) ROHM has used reasonable care to ensur the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 12) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 13) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 14) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations. More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

http://www.rohm.com/contact/